

## LE 230 Homework : Ordinary Differential Equations

**Please show all details of your solutions.**

7-1. Let  $R = 1 \text{ k}\Omega$ ,  $C = 1 \text{ }\mu\text{F}$ , find

(a)  $v_C(t)$  for a series  $RC$  circuit with  $v_C(0^-)=0$  and voltage source  $V_s(0^+) = u(t)$  V.

(b)  $v_C(t)$  for a parallel  $RC$  circuit with  $v_C(0^-)=0$  and current source  $I_s(0^+) = u(t)$  A.

using Euler, mid-point, RK2, RK4 methods.

7-2. Let  $R = 1 \text{ }\Omega$ ,  $L = 1 \text{ mH}$ , find

(c)  $i_L(t)$  for a series  $RL$  circuit with  $i_L(0^-)=0$  and voltage source  $V_s(0^+) = u(t)$ .

(d)  $i_L(t)$  for a parallel  $RL$  circuit with  $i_L(0^-)=0$  and current source  $I_s(0^+) = u(t)$ .

using Euler, mid-point, RK2, RK4 methods.

7-3. Repeat problem 7-1 with source changed to triangular pulse of height 1 and width 1 ms.

7-4. Repeat problem 7-2 with source changed to triangular pulse of height 1 and width 1 ms.

7-5. Let  $R = 2 \text{ k}\Omega$ ,  $L = 0.1 \text{ H}$ ,  $C = .1 \text{ }\mu\text{F}$ , find

$v_C(t)$  for a series  $RLC$  circuit with  $v_C(0^-)=0$ ,  $i_C(0^-) = 0$  and voltage source  $V_s(0^+) = u(t)$

using Euler, RK2, RK4 methods.

Then repeat the problem with  $C$  changed to  $1 \text{ }\mu\text{F}$  and  $10 \text{ nF}$ , respectively.

7-6. Repeat problem 7-5 with source changed to triangular pulse of height 1 and width 4 ms.

7-7. Let  $R = 0.8 \text{ k}\Omega$ ,  $L = 0.1 \text{ H}$ ,  $C = .1 \text{ }\mu\text{F}$ , find

$i_L(t)$  for a parallel  $RLC$  circuit with  $v_L(0^-)=0$ ,  $i_L(0^-) = 0$  and current source  $I_s(0^+) = u(t)$ .

using Euler, RK2, RK4 methods.

Then repeat the problem with  $C$  changed to  $1 \text{ }\mu\text{F}$  and  $10 \text{ nF}$ , respectively.

7-8. Repeat problem 7-7 with source changed to triangular pulse of height 1 and width 4 ms.

**NOTE:**

1.  $u(t-a)$  denotes the unit step function given by:

$$u(t-a) = \begin{cases} 1 & t \geq a \\ 0 & t < a \end{cases}$$

2. Continue computations until systems reach “steady” states.