

ASYNCHRONOUS SEQUENTIAL CIRCUITS

- ❖ Sequential circuits that are not synchronized by a clock – Asynchronous circuits
- ❖ Analysis of Asynchronous circuits
- ❖ Synthesis of Asynchronous circuits
- ❖ Hazards that cause incorrect behavior of a circuit



ASYNCHRONOUS SEQUENTIAL CIRCUITS

❖ Synchronous sequential circuits

- state variables : F/Fs
- controlled by a clock
- operate in pulse mode

❖ Asynchronous sequential circuits

- do not operate in synchronous with *clock signal*.
- do not use F/Fs to represent state variables
- Changes in state are dependent on whether each of inputs to the circuit has the logic level 0 or 1 at any given time

❖ To achieve reliable operation

- the inputs to the circuit must change one at a time
- there must be sufficient time between the changes in input signals to allow the circuit to reach a stable state
- A circuit that adheres to these constraints is said to operate in the *fundamental* mode

ADVANTAGES OF ASYNCHRONOUS CIRCUITS

- ❖ No clock skew (clock signal arrives at different time)
- ❖ Lower power (Synchronous : clock signal must be present every time and everywhere.
- ❖ Average-case performance VS worst-case performance
- ❖ Easing of global timing issues
- ❖ Partial optimization
- ❖ Better external input handling



DRAWBACKS

- ❖ More difficult to design
- ❖ Concerns for hazards and glitches
- ❖ Unsure about faster performance



WHY ASYNCHRONOUS CIRCUITS ?

- ❖ Used when speed of operation is important
 - Response quickly without waiting for a clock pulse
- ❖ Used in small independent systems
 - Only a few components are required
- ❖ Used when the input signals may change independently of internal clock
 - Asynchronous in nature
- ❖ Used in the communication between two units that have their own independent clocks
 - Must be done in an asynchronous fashion



MODE OF OPERATIONS

❖ Steady-state condition:

- Current states and next states are the same
- Difference between Y and y will cause a transition


❖ Fundamental mode:

- No simultaneous changes of two or more variables
- The time between two input changes must be longer than the time it takes the circuit to a stable state
- The input signals change one at a time and only when the circuit is in a stable condition Fundamental Mode

❖ Pulse Mode:

- the inputs and outputs are represented by pulses.
- only one input is allowed to have pulse present at any time.
- Similar to synchronous sequential circuits except without a clock signal.

GENERAL BLOCK DIAGRAM

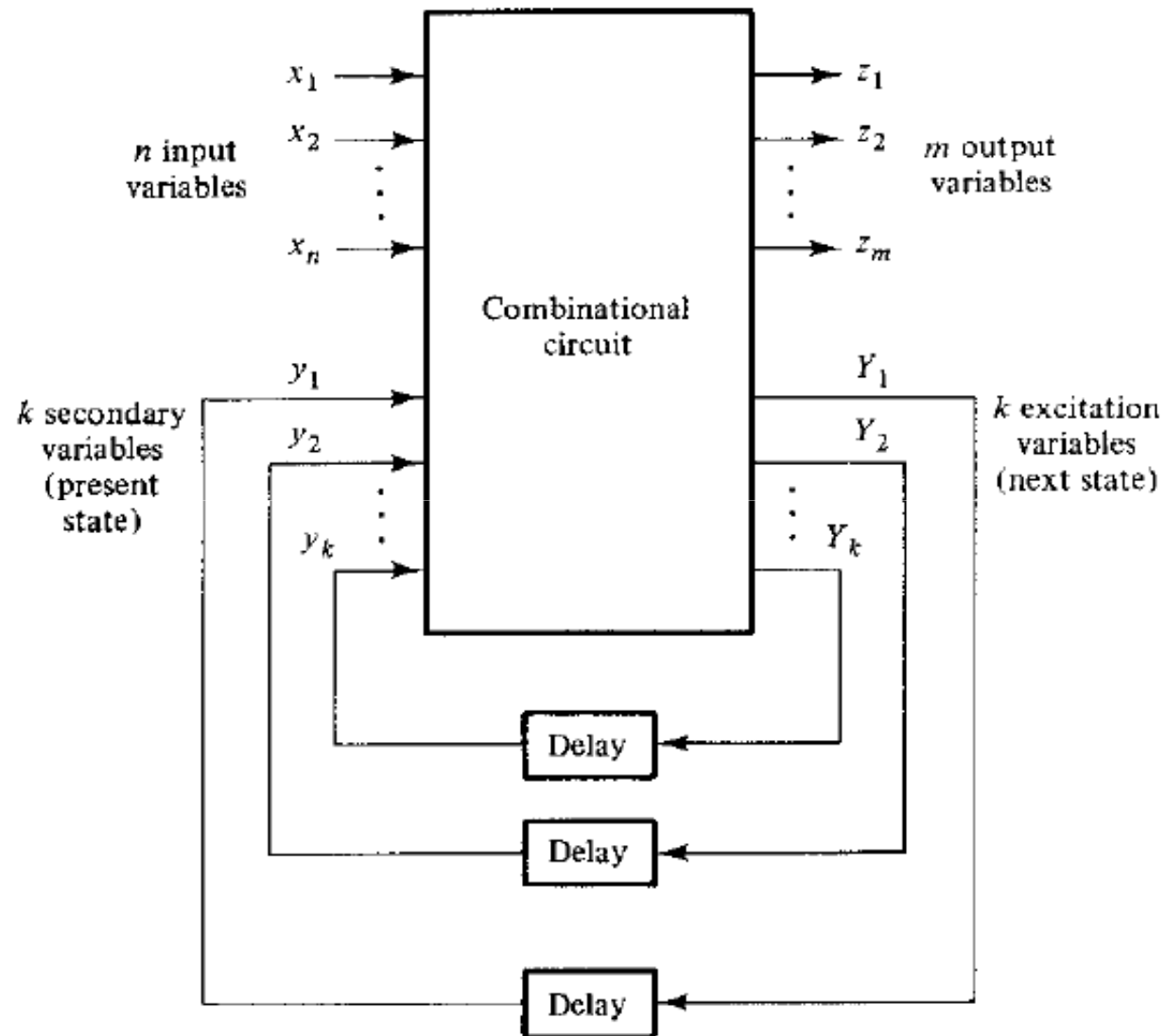

TERMINOLOGY

❖ Asynchronous circuits

- state table -> flow table

- state-assigned table -> transition table or excitation table


❖ will use the term flow table and excitation table



STEPS IN THE ANALYSIS PROCESS

- ❖ Each feedback path is cut
 - A delay element is inserted at the point where the cut is made
 - A cut can be made anywhere in a particular loop formed by feedback connection, as long as there is only one cut per (state variable) loop
- ❖ Next-state and output expressions are derived from the circuit
- ❖ The excitation table is derived
- ❖ A flow table is obtained
- ❖ A corresponding state diagram is derived from the flow table if desired

ASYNCHRONOUS BEHAVIOR OF SR-LATCH

 

$$Y = \overline{(y + S) + R}$$

$$= \overline{y' S' + R} = (y + S) R'$$

Stable state: given inputs, if a circuit reaches a state and remains in that state, then the state is said to be “stable”.

Present state <i>y</i>	Next state			
	<i>SR</i> = 00	01	10	11
	<i>Y</i>	<i>Y</i>	<i>Y</i>	<i>Y</i>
0	0	0	1	0
1	1	0	1	0


(b) State-assigned table

Circles denote “stable” states, i.e., state “unchanged”.

MOORE FSM MODEL

Present state	Next state				Output Q
	$SR = 00$	01	10	11	
A	\textcircled{A}	\textcircled{A}	B	\textcircled{A}	0
B	\textcircled{B}	A	\textcircled{B}	A	1

(a) State table

 


(b) State diagram

$$\begin{aligned}
 Y &= \overline{(y + S)} + R \\
 &= \overline{y'S' + R} \\
 &= (y + S)R' \\
 Q &= y
 \end{aligned}$$

MEALY FSM

Present state	Next state				Output, Q			
	$SR = 00$	01	10	11	00	01	10	11
A	(A)	(A)	B	(A)	0	0	–	0
B	(B)	A	(B)	A	1	–	1	–

(a) State table

 


(b) State diagram

Unspecified output :

At state A: input 10 changes to state B,
 $Y=1$, $Q=1$ after reaching state B.

No need to change it beforehand.

GATED D-LATCH

 

$$\begin{aligned}
 Y &= \overline{\overline{CD} \cdot \overline{CD'} \cdot y} \\
 &= \overline{(C' + D') \cdot (C' + D) \cdot y} \\
 &= \overline{(C' + D') \cdot ((C' + D) + y')} \\
 &= \overline{(C' + D') \cdot (CD' + y')} \\
 &= CD + C'y + Dy
 \end{aligned}$$

$$Q = y$$

Consensus
term


Present state y	Next state				Q
	$CD = 00$	01	10	11	
	Y	Y	Y	Y	
0	0	0	0	1	0
1	1	1	0	1	1

(b) Excitation table

GATED D-LATCH (2)


Present state	Next state				Q
	$CD = 00$	01	10	11	
A	\textcircled{A}	\textcircled{A}	\textcircled{A}	B	0
B	\textcircled{B}	\textcircled{B}	A	\textcircled{B}	1

(c) Flow table

 

(d) State diagram

MASTER-SLAVE D FLIP-FLOP

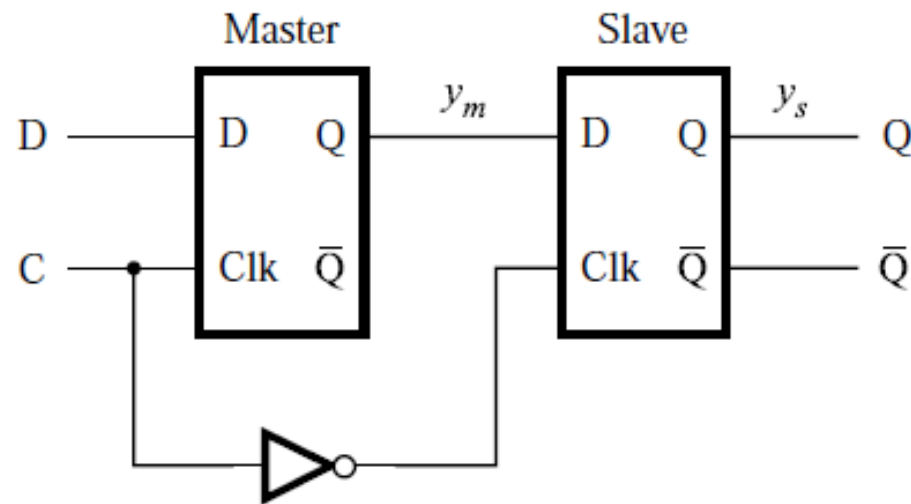

$$Y_m = CD + C' y_m$$

$$Y_s = C' y_m + Cy_s$$

$$Q = y_s$$

Present state $y_m y_s$	Next state				Output Q
	$CD = 00$	01	10	11	
	$Y_m Y_s$				
00	00	00	00	10	0
01	00	00	01	11	1
10	11	11	00	10	0
11	11	11	01	11	1

(a) Excitation table


MASTER-SLAVE D FLIP-FLOP (2)

Present state	Next state				Output Q
	$CD = 00$	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	S1	(S2)	S4	1
S3	S4	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

(b) Flow table

Present state	Next state				Output Q
	$CD = 00$	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	—	(S2)	S4	1
S3	—	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1


(c) Flow table with unspecified entries

 

Unspecified entries :

At state S2: stable with input $CD=10$. Thus, cannot achieve $CD=01$. (2 inputs cannot change at the same time.)

FURTHER EXAMPLE

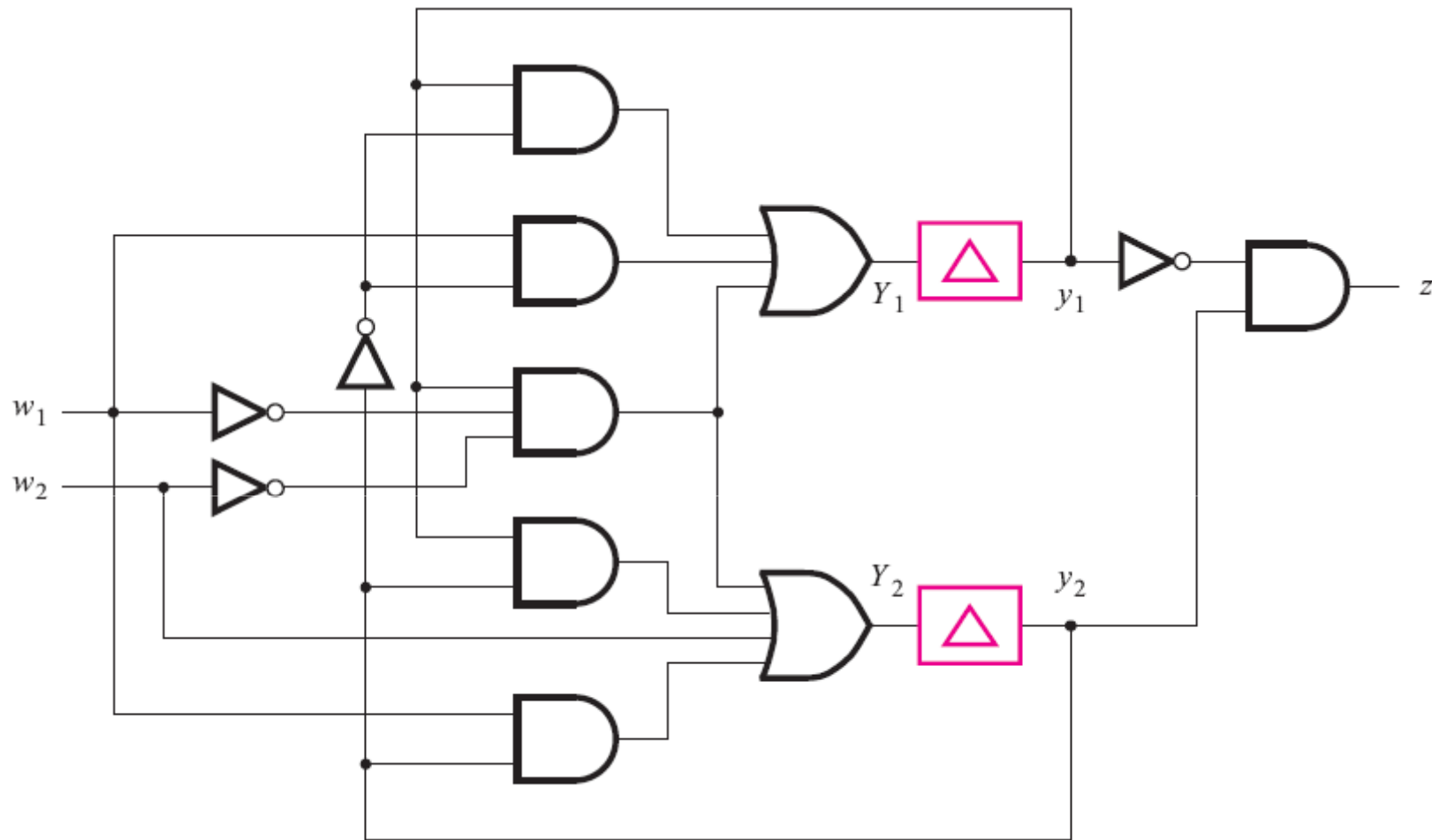

$$Y_1 = y_1 y_2' + w_1 y_2' + w_1' w_2' y_1$$

$$Y_2 = y_1 y_2 + w_1 y_2 + w_2 + w_1' w_2' y_1; z = y_1' y_2$$

FURTHER EXAMPLE (2)

Present state $y_2 y_1$	Next state				Output z
	$w_2 w_1 = 00$	01	10	11	
	$Y_2 Y_1$	$Y_2 Y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
00	⓪⓪	01	10	11	0
01	11	⓪1	11	11	0
10	00	⓪0	⓪0	⓪0	1
11	⓪1	10	10	10	0

(a) Excitation table


Present state	Next state				Output z
	$w_2 w_1 = 00$	01	10	11	
A	⓪	B	C	D	0
B	D	⓪	D	D	0
C	A	⓪	⓪	⓪	1
D	⓪	C	C	C	0

(b) Flow table

FURTHER EXAMPLE (3)

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	B	C	—	0
B	D	(B)	—	D	0
C	A	(C)	(C)	(C)	1
D	(D)	C	C	C	0

 Unspecified entries :
 At state B: stable with input $w_2w_1=01$. Thus, cannot achieve $w_2w_1=10$. (2 inputs cannot change at the same time.)




SYNTHESIS OF ASYNCHRONOUS CIRCUITS

the same basic steps used to synthesize the synchronous circuits


1. Devise a state diagram for an FSM
 2. Derive the flow table and reduce the number of states if Possible
 3. Perform the state assignment and derive the excitation table
 4. Obtain the next-state and output expressions
 5. Construct a circuit that implements these expressions
- ❖ Reverse of Analysis

 EXAMPLE: SERIAL PARITY GENERATOR

- ❖ input w : pulses are applied to w
- ❖ output z
- ❖ $z=1$ if the number of previously applied pulses is odd



EXAMPLE: SERIAL PARITY GENERATOR (2)

 

(a) State diagram

Present State	Next state		Output z
	$w = 0$	$w = 1$	
A	(A)	B	0
B	C	(B)	1
C	(C)	D	1
D	A	(D)	0

(b) Flow table

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	⓪⓪	01	0
01	10	⓪1	1
10	⓪10	11	1
11	00	⓪11	0

(a) Poor state assignment

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment

STATE ASSIGNMENT

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

(a) Poor state assignment

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment

- ❖ State assignment (a) has a major flaw
- ❖ state D = 11 : $w=0 \rightarrow$ state A
- ❖ $y_2y_1=11 \rightarrow y_2y_1=00$
- ❖ the values of the next-state variables determined by the networks of logic gates with varying delays
 - suppose y_1 changes first
 - ❖ $y_2y_1=10 \rightarrow$ state C(10)
 - ❖ state C is stable when $w=0$
 - suppose y_2 changes first
 - ❖ $y_2y_1=01 \rightarrow$ state B (01)
 - ❖ try to change to $y_2y_1=10$ when $w=0$
 - ❖ if y_1 changes first, $y_2y_1=00$
- *race condition occurs*

RACE CONDITION

A race is said to occur if between next set of states S_q **and present states** s_q , there are two or more bits change (two or more latches undergoes change in Q output) at the memory or delay section.

Race condition arises due to variable number of delays of different latches, which lead to intermediate states.




NEXT-STATE EQ'S & CIRCUIT DIAGRAM

$$Y_1 = wy_2' + w' y_1 + y_1 y_2'$$


$$Y_2 = wy_2 + w' y_1 + y_1 y_2$$

$$z = y_1$$

Hazard prevention


 


Synchronous Solution

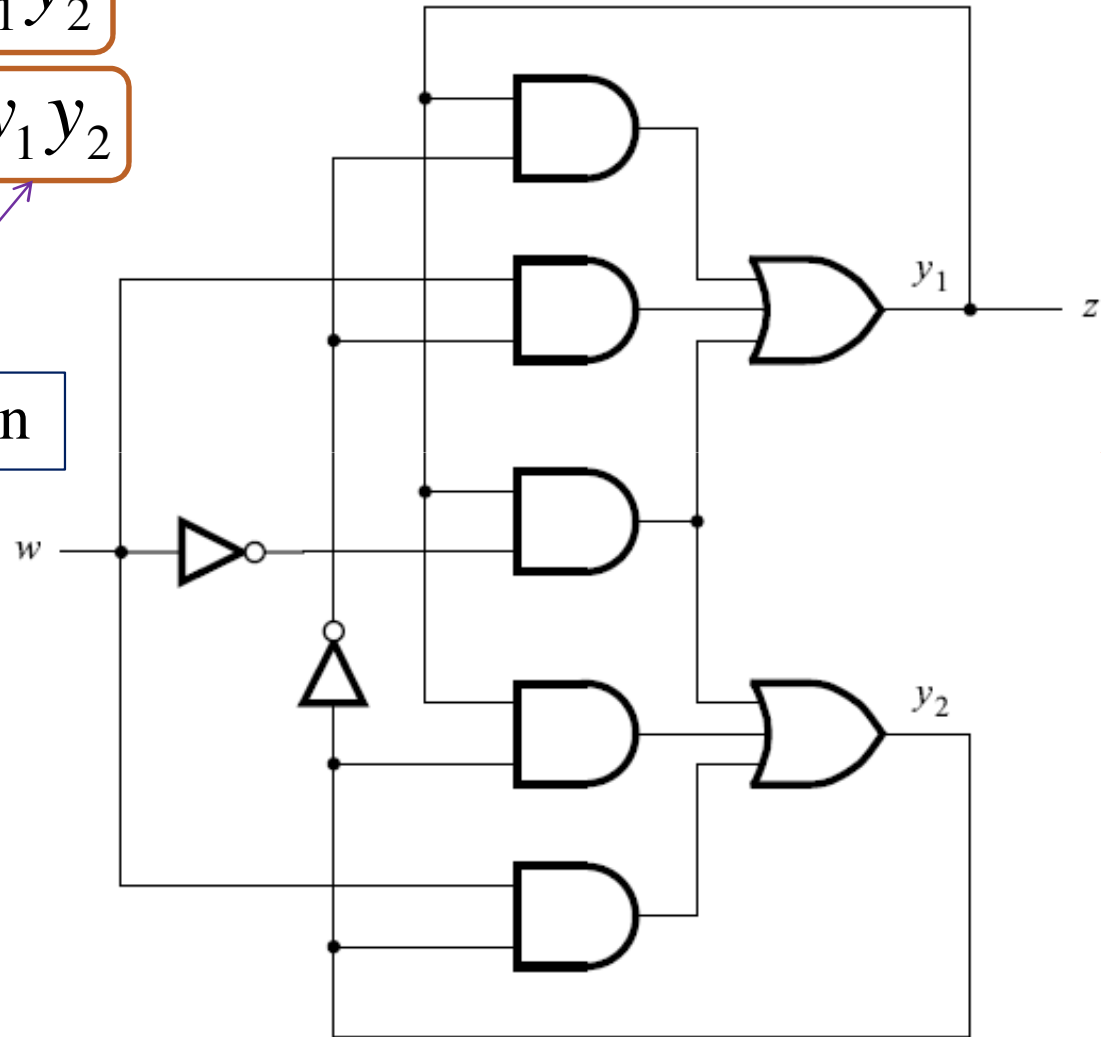

MODULO-4 UP COUNTER

  - ❖ Input w: 1 cause $A \rightarrow B$, and stay there.
- ❖ $w=0$ cause $B \rightarrow C$ and so on



FLOW TABLE & EXCITATION TABLE

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	(A)	B	0
B	C	(B)	1
C	(C)	D	1
D	E	(D)	2
E	(E)	F	2
F	G	(F)	3
G	(G)	H	3
H	A	(H)	0

(a) Flow table

Present state $y_3y_2y_1$	Next state		Output z_2z_1
	$w = 0$	$w = 1$	
	$Y_3Y_2Y_1$		
000	000	001	00
001	011	001	01
011	011	010	01
010	110	010	10
110	110	111	10
111	101	111	11
101	101	100	11
100	000	100	00

(b) Excitation table

NEXT STATE & OUTPUT EQ'S

$$Y_1 = w' y_1 + w y_2 y_3 + w y_2' y_3' + y_1 y_2 y_3 + y_1 y_2' y_3'$$

$$Y_2 = w y_2 + w' y_1 y_3' + y_1' y_2 + y_2 y_3'$$

$$Y_3 = w y_3 + y_1 y_3 + y_1' y_2 w' + y_2 y_3$$

$$z_1 = y_1$$

$$z_2 = y_1 y_3 + y_1' y_2$$

❖ Exercise: Draw the circuit diagram.

STATE REDUCTION

- ❖ For simpler implementation (fewer FF's and so on)
- ❖ Two step approach
 - Partitioning (Same as the synchronous case)
 - ❖ Equivalent states : equivalent k -successors and equivalent stable next-state with same input.
 - Use **merger diagram**

COMPATIBILITY OF STATES

Definition: *Two states (rows in a flow table), S_i and S_j , are said to be compatible if there are no state conflicts for any input valuation. Thus for each input valuation, one of the following conditions must be true:*

- ❖ *both S_i and S_j have the same successor, or*
- ❖ *both S_i and S_j are stable, or*
- ❖ *the successor of S_i or S_j , or both, is unspecified.*

Moreover, both S_i and S_j must have the same output whenever specified.

COMPATIBLE STATES EXAMPLE

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	H	B	—	0
B	F	—	(B)	C	0
C	—	H	—	(C)	1
D	A	(D)	—	E	1
E	—	D	G	(E)	1
F	(F)	D	—	—	0
G	F	—	(G)	—	0
H	—	(H)	—	E	0


Compatible pairs:
 (A,H), (B,F),
 (B,G), (D,E),
 (F,G), (G,H).

Primitive Flow Table

MERGER DIAGRAM


- ❖ Used to represent the *compatibility* relationship.
- ❖ Procedure
 - Each row of the flow table is represented as a point, labeled by the name of the row.
 - A line is drawn connecting any two points that correspond to compatible states (rows).
- ❖ The reduced flow table can be derived from the merger diagram by choosing the “best” merging possibility.

 MERGER DIAGRAM FOR PREVIOUS COMPATIBLE STATES EXAMPLE



Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	Ⓐ	Ⓐ	B	D	0
B	Ⓑ	D	Ⓑ	C	0
C	—	A	—	Ⓒ	1
D	A	Ⓓ	B	Ⓓ	1

Reduced Moore-type Flow Table

 

Complete Merger Diagram (Include Mealy-type FSM)
Black line : Moore-type

STATE REDUCTION PROCEDURE

1. Use the partitioning procedure to eliminate the equivalent states in a primitive flow table.
2. Construct a merger diagram for the resulting flow table.
3. Choose subsets of compatible states that can be merged, trying to minimize the number of subsets needed to cover all states. Each state must be included in only one of the chosen subsets.
4. Derive the reduced flow table by merging the rows in chosen subsets.
5. Repeat steps 2 to 4 to see whether further reductions are possible.

STATE REDUCTION EXAMPLE 1

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	F	C	—	0
B	A	(B)	—	H	1
C	G	—	(C)	D	0
D	—	F	—	(D)	1
E	G	—	(E)	D	1
F	—	(F)	—	K	0
G	(G)	B	J	—	0
H	—	L	E	(H)	1
J	G	—	(J)	—	0
K	—	B	E	(K)	1
L	A	(L)	—	K	1

$$P_1 = (AG)(BL)(C)(D)(E)(F)(HK)(J)$$


$$P_2 = (A)(G)(BL)(C)(D)(E)(F)(HK)(J)$$

$$P_3 = P_2$$



Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	F	C	—	0
B	A	(B)	—	H	1
C	G	—	(C)	D	0
D	—	F	—	(D)	1
E	G	—	(E)	D	1
F	—	(F)	—	H	0
G	(G)	B	J	—	0
H	—	B	E	(H)	1
J	G	—	(J)	—	0

STATE REDUCTION EXAMPLE 1 (2)

 

Merger Diagram

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	(A)	C	B	0
B	A	(B)	D	(B)	1
C	G	—	(C)	D	0
D	G	A	(D)	(D)	1
G	(G)	B	(G)	—	0

Reduced Flow Table

STATE REDUCTION EXAMPLE 1 (3)

A
•

B
•

D
•

C
•

G
•



Merger Diagram for reduced flow table


Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	(A)	C	B	0
B	A	(B)	D	(B)	1
C	(C)	B	(C)	D	0
D	C	A	(D)	(D)	1

Finalized Flow Table



STATE REDUCTION EXAMPLE 2

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	B	C	—	0
B	F	(B)	—	H	0
C	F	—	(C)	H	0
D	(D)	G	C	—	1
E	A	(E)	—	H	0
F	(F)	E	C	—	0
G	D	(G)	—	H	0
H	—	G	C	(H)	1

 


$$P_1 = (AF)(BEG)(C)(D)(H)$$

$$P_2 = (AF)(BE)(G)(C)(D)(H)$$

$$P_3 = P_2$$

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	B	C	—	0
B	A	(B)	—	H	0
C	A	—	(C)	H	0
D	(D)	G	C	—	1
G	D	(G)	—	H	0
H	—	G	C	(H)	1

STATE REDUCTION EXAMPLE 2 (2)

 

Merger Diagram

Present state	Next state				Output z			
	$w_2w_1 = 00$	01	10	11	00	01	10	11
A	(A)	(A)	(A)	D	0	0	0	—
D	(D)	(D)	A	(D)	1	0	—	1


Reduced Flow Table

AN ASYNCHRONOUS VENDING MACHINE

Specification A candy vending machine with

- accepts only nickels and dimes
- 10 cents for 1 candy
- No change given.

Initial State
Diagram

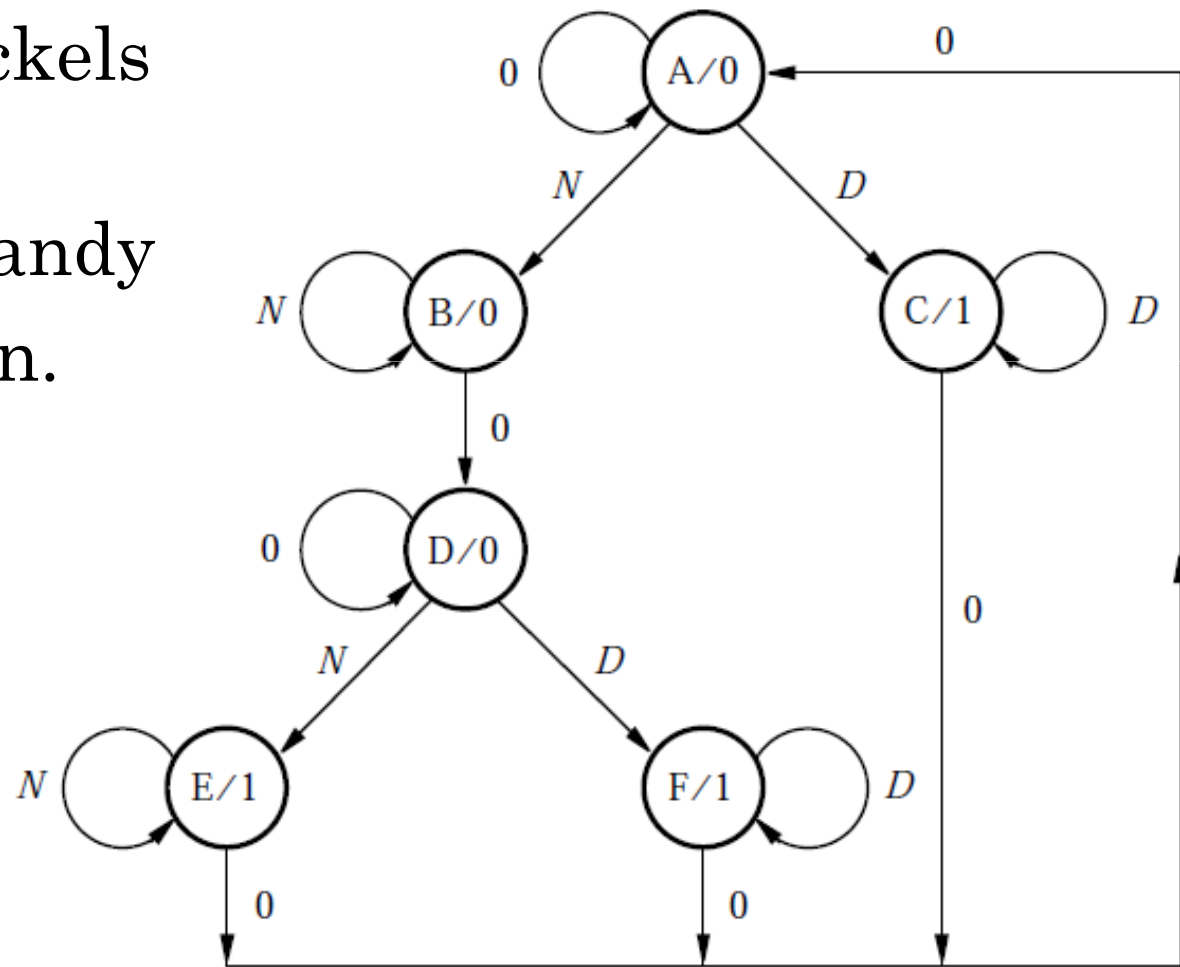


AN ASYNCHRONOUS VENDING MACHINE (2)

Present State	Next state				Output z
	$DN = 00$	01	10	11	
A	(A)	B	C	—	0
B	D	(B)	—	—	0
C	A	—	(C)	—	1
D	(D)	E	F	—	0
E	A	(E)	—	—	1
F	A	—	(F)	—	1

$$P_1 = (AD)(B)(CF)(E)$$


$$P_2 = (A)(D)(B)(CF)(E)$$

$$P_3 = P_2$$

 

Present state	Next state				Output z
	$DN = 00$	01	10	11	
A	(A)	B	C	—	0
B	D	(B)	—	—	0
C	A	—	(C)	—	1
D	(D)	E	C	—	0
E	A	(E)	—	—	1

AN ASYNCHRONOUS VENDING MACHINE (3)

 

Merger Diagram

Present state	Next state					Output z
	DN	$= 00$	01	10	11	
A		(A)	B	C	—	0
B		D	(B)	—	—	0
C		A	(C)	(C)	—	1
D		(D)	C	C	—	0

Reduced Flow Table

STATE ASSIGNMENT

- ❖ To achieve reliable operation of the circuit, the state variables should change their values one at a time in controlled fashion. This can prevent the race.
- ❖ Hamming distance : the number of different bits, e.g., 0100,0011 → distance 3.
- ❖ Ideal state assignment: Hamming distance of 1 for all transitions from one stable state to another. (may not be possible!!!)

TRANSITION DIAGRAM



- ❖ Or *state-adjacency diagram*, used for depicting the state transitions to provide a convenient aid in searching for a suitable state assignment.
- ❖ A good state assignment results if the transition diagram does not have any **diagonal** paths.
- ❖ Condition: Must be possible to *embed* the transition diagram onto a *k-dimensional cube*



TRANSITIONS EXAMPLE


Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

(a) Poor state assignment

  

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment

 

RACE CONDITION

- ❖ A race condition occurs in an asynchronous circuit when 2 or more state variables change in response to a change in the value of a circuit input.
- ❖ Unequal circuit delays may imply that the 2 or more state variables may not change simultaneously – this can cause a problem.
- ❖ Assume two state variables change...
 - If the circuit reaches the same final, stable state regardless of the order in which the state variables change, then the race is **non-critical**.
 - If the circuit reaches a different final, stable state depending on the order in which the state variables change, then the race is **critical**.
- ❖ We need to avoid critical races for predictability and to ensure our circuit does the intended function!

NON-CRITICAL RACE

- ❖ Assume current state is 00, and input changes from 0 \rightarrow 1. This requires y_1y_2 to change from 00 \rightarrow 11.

		x	
		0	1
curr state	y_1y_2	00	11
	01	00	01
	11	00	01
	10	00	11

- ❖ Depending on circuit delays, several possible transition sequences:
 - 00 \rightarrow 11 \rightarrow 01 (simultaneous change for y_1 and y_2).
 - 00 \rightarrow 01 (y_2 changes first).
 - 00 \rightarrow 10 \rightarrow 11 \rightarrow 01 (y_1 changes first)
- ❖ In all cases, we end up in the same stable state, so the race is **non-critical**.

CRITICAL RACE

- ❖ Assume current state is 00, and input changes from 0->1. This requires y_1y_2 to change from 00->11.

	y_1y_2	x	
		0	1
curr state	00	00	11
	01	00	11
	11	00	11
	10	00	10

- ❖ Possible transition sequences:
 - 00->11 (y_1 and y_2 change simultaneously)
 - 00->01->11 (y_2 changes first)
 - 00->10 (y_1 changes first)
- ❖ So, depending on which state variable changes first, we can get into a **different stable state** – the race is critical.

ADDITIONAL EXAMPLE

	x	
	0	1
y_1y_2		
00	00	11
01		11
11		11
10		11

(a) Possible transitions:

$00 \rightarrow 11$
 $00 \rightarrow 01 \rightarrow 11$
 $00 \rightarrow 10 \rightarrow 11$

Non-critical

	x	
	0	1
y_1y_2		
00	00	11
01		01
11		01
10		11

(b) Possible transitions:

$00 \rightarrow 11 \rightarrow 01$
 $00 \rightarrow 01$
 $00 \rightarrow 10 \rightarrow 11 \rightarrow 01$

	x	
	0	1
y_1y_2		
00	00	11
01		01
11		11
10		10

(a) Possible transitions:

$00 \rightarrow 11$
 $00 \rightarrow 01$
 $00 \rightarrow 10$

	x	
	0	1
y_1y_2		
00	00	11
01		11
11		11
10		10

(b) Possible transitions:

$00 \rightarrow 11$
 $00 \rightarrow 01 \rightarrow 11$
 $00 \rightarrow 10$

Critical

CYCLES

- ❖ A cycle occurs when a circuit goes through a unique sequence of **unstable** states.

	x	
	0	1
$y_1 y_2$		
00	(00)	01
01		11
11		10
10		(10)

(a) State transition:

00 \rightarrow 01 \rightarrow 11 \rightarrow 10

	x	
	0	1
$y_1 y_2$		
00	(00)	01
01		11
11		(11)
10		(10)

(b) State transition:

00 \rightarrow 01 \rightarrow 11


	x	
	0	1
$y_1 y_2$		
00	(00)	01
01		11
11		10
10		01

(c) Unstable

\rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow

INSTABILITY

 - ❖ When $x_1x_2=11$, $y=1$, then $Y=0$, $Y \neq y$.
- ❖ Then $y=0 \rightarrow Y=1$, $Y \neq y$.
- ❖ If each gate has a 5-ns propagation delay, $Y=0$ for 10 ns, and $Y=1$ for 10 ns, resulting in 50-MHz clock signal!



(a) Logic diagram

		x_1x_2			
		00	01	11	10
y	0	0	1	1	0
	1	0	1	0	0


(b) Transition table

RACE-FREE STATE ASSIGNMENT

- ❖ Can prevent races (pre-emptive) by performing state assignment such that transitions from **one stable state to another stable state only require one state variable to change at a time.**

curr state	next state	
	x=0	x=1
a	a	b
b	c	b
c	c	d
d	a	d

Flow Table

 

BAD
State Assignment

Good
State Assignment


METHOD ONE FOR RACE FREE STATE ASSIGNMENT

- ❖ Given a flow table, try and “embed” the symbolic states into the co-ordinates of a “n-dimensional” cube such that the path from stable state to stable state:
 - Is direct along a single edge of the cube, or
 - Goes through newly introduced unstable states along edges of the cube.



METHOD ONE EXAMPLE

curr state	next state			
	x1x2=00	x1x2=01	x1x2=10	x1x2=11
a	a	a	c	b
b	a	b	d	b
c	c	b	c	d
d	c	a	d	d

 



❖ Can attempt to embed 4 states into a 2-dimensional cube and draw the transition diagram:

➤ No state assignment that has only one state variable changing at a time.

METHOD ONE EXAMPLE (CONT)


❖ Solution is to introduce additional, unstable states and use them as “intermediate” states during transitions.

  ➤ i.e., embed the 4-states into the corners of a 3-dimensional cube.



METHOD ONE EXAMPLE (CONT)

 
- ❖ All transitions are made properly by introducing extra unstable states (Note: the new extra states are always unstable!!!):



EXAMPLE : RACE-FREE FLOW TABLE

- ❖ Can now see the original flow table, and an expanded flow table (extra unstable states) that has a race-free state assignment (see previous slide!):

curr state	next state			
	x1x2=00	x1x2=01	x1x2=10	x1x2=11
a	a	a	c	b
b	a	b	d	b
c	c	b	c	d
d	c	a	d	d

 

curr state	next state			
	x1x2=00	x1x2=01	x1x2=10	x1x2=11
a	a	a	c	b
b	a	b	e	b
c	c	b	c	g
d	g	a	d	d
e	-	-	d	-
f	-	b	-	-
g	c	-	-	d

METHOD TWO FOR RACE FREE STATE ASSIGNMENT

- ❖ Method useful for flow tables with ≤ 4 states.
- ❖ Replace a state with multiple (two) equivalent states
 - Note: Outputs must be the same for the **equivalent** states!!!



METHOD TWO EXAMPLE

- ❖ Consider the following flow table, and another (larger table) with equivalent states:


curr state	next state				output
	x1x2=00	x1x2=01	x1x2=10	x1x2=11	
a	a	a	c	b	0
b	a	b	d	b	1
c	c	b	c	d	0
d	c	a	d	d	1

curr state	next state				output
	x1x2=00	x1x2=01	x1x2=10	x1x2=11	
a1	a1	a1	c1	b1	0
a2	a2	a2	a1	b2	0
b1	a1	b1	b2	b1	1
b2	a2	b2	d2	b2	1
c1	c1	c2	c1	d1	0
c2	c2	b1	c2	d2	0
d1	c1	d2	d1	d1	1
d2	c2	d1	d2	d2	1

- ❖ The flow table with equivalent states permits a race free state assignment.
- ❖ We can see this by looking at the states on a 3-dimensional cube.

METHOD TWO EXAMPLE (CONT)

curr state	next state				output
	x1x2=00	x1x2=01	x1x2=10	x1x2=11	
a1	a1	a1	c1	b1	0
a2	a2	a2	a1	b2	0
b1	a1	b1	b2	b1	1
b2	a2	b2	d2	b2	1
c1	c1	c2	c1	d1	0
c2	c2	b1	c2	d2	0
d1	c1	d2	d1	d1	1
d2	c2	d1	d2	d2	1

 

❖ With equivalent states, we always have 1 of the 2 equivalent states directly adjacent to every other state!

METHOD THREE FOR RACE-FREE STATE ASSIGNMENT


- ❖ Can use the idea of one-hot encoding to get a race free state assignment...
- ❖ Given n -states, let the i^{th} state be encoded as $0...010..0$ where the 1 is in the i^{th} location.
- ❖ For a transition from i^{th} stable state to j^{th} stable state, introduce unstable state with encoding $0..010..010..0$ where the 1s are in the i^{th} and j^{th} position.



METHOD THREE EXAMPLE

- ❖ Consider the following flow table, with one-hot state assignment:
- ❖ Look for transitions and introduce new unstable states, as required using one-hot encoding scheme.

	curr state	next state			
		x1x2=00	x1x2=01	x1x2=10	x1x2=11
0001	a	a	a	c	b
0010	b	a	b	d	b
0100	c	c	b	c	d
1000	d	c	a	d	d

 

	curr state	next state			
		x1x2=00	x1x2=01	x1x2=10	x1x2=11
0001	a	a	a	e	f
0010	b	f	b	g	b
0100	c	c	h	c	i
1000	d	c	j	d	d
0101	e	-	-	c	-
0011	f	a	-	-	b
1010	g	-	-	d	-
0110	h	-	b	-	-
1100	i	c	-	-	d
1001	i	-	a	-	-

ASYNCHRONOUS SEQUENTIAL CIRCUITS SUMMARY

❖ Analysis:

- From the logic diagram, determine input, output, state variable.
- Derive Boolean functions.
- Obtain excitation table, flow table, state diagram.

❖ Synthesis (Design):

- Determine state diagram and primitive flow table.
- Reduce states if possible.
- Assign states and obtain excitation table.
- Derive Boolean functions and design circuit.